

---

# EECS 16A      Designing Information Devices and Systems I

## Fall 2022      Discussion 9A

---

### Mid Semester Survey


Please fill out the mid semester survey: <https://tinyurl.com/midsemester16a>

We highly appreciate your feedback!


### 1. Capacitance Equivalence

For the structures shown below, assume that the plates have a depth  $L$  into the page and a width  $W$  and are always a distance  $d$  apart. The dielectric between the plates has absolute permittivity  $\epsilon$ . For the following calculations, assume the capacitance is purely parallel plate, i.e. ignore fringing field effects.

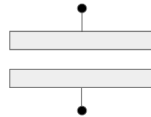
- (a) What is the capacitance of the structure shown below?



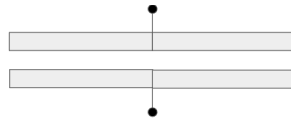
- (b) Suppose that we take two such structures and put them next to each other as shown below. What is the capacitance of this new structure?



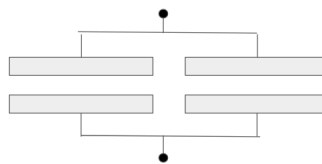
- (c) Now suppose that rather than connecting them together as shown above, we connect them with an ideal wire as shown below. What is the capacitance of this structure?



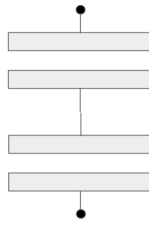- (d) Suppose that we now take two capacitors and connect them as shown below. What is the capacitance of the structure?



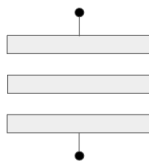
- (e) What is the capacitance of the structure shown below?




## 2. Series And Parallel Capacitors

Derive  $C_{eq}$  for the following circuits.

(a)

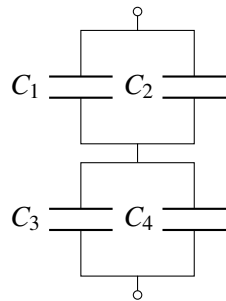


(b)

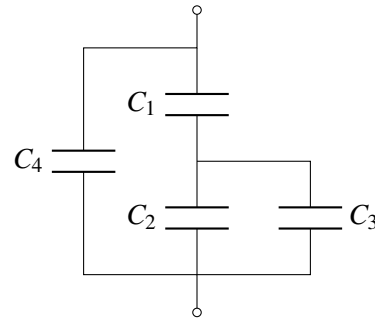
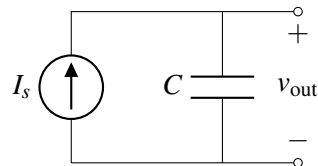
## 3. Current Sources And Capacitors

Given the circuit below, find an expression for  $v_{out}(t)$  in terms of  $I_s$ ,  $C$ ,  $V_0$ , and  $t$ , where  $V_0$  is the initial voltage across the capacitor at  $t = 0$ .



Then plot the function  $v_{out}(t)$  over time on the graph below for the following conditions detailed below. Use the values  $I_s = 1\text{mA}$  and  $C = 2\mu\text{F}$ .

- (a) Capacitor is initially uncharged, with  $V_0 = 0$  at  $t = 0$ .
- (b) Capacitor has been charged with  $V_0 = +1.5\text{V}$  at  $t = 0$ .
- (c) **Practice:** Swap this capacitor for one with half the capacitance  $C = 1\text{ }\mu\text{F}$ , which is initially uncharged, with  $V_0 = 0$  at  $t = 0$ .

HINT: Recall the calculus identity  $\int_a^b f'(x)dx = f(b) - f(a)$ , where  $f'(x) = \frac{df}{dx}$ .

