

# EECS 16A Designing Information Devices and Systems I

## Spring 2023 Discussion 9B

*Note to students:*


In this worksheet, we are using comparators (denoted by the little square wave within the op-amp symbol), which are distinct from op-amps that we will be covering in the coming weeks. While it is true op-amps can be used as comparators, this is not practical since comparators are faster than op amps, consume less power, and occupy smaller area. Op-amps are designed for signal amplifications whereas comparators are specifically dedicated to signal comparison (more on this later).

Here is the inherent logic of a comparator:

- If  $V_+ > V_-$ , then  $V_{out} = V_{DD}$  (positive supply rail)
- If  $V_+ < V_-$ , then  $V_{out} = V_{SS}$  (negative supply rail)
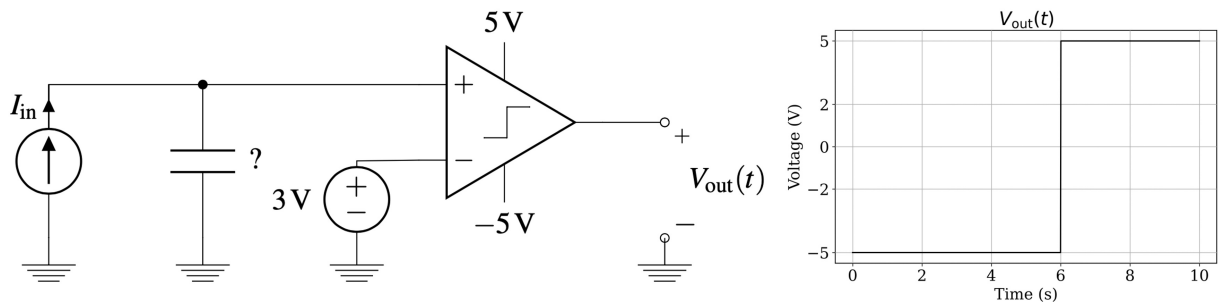
### 1. Comparators

We want to find the value of an unknown capacitor using the comparator outputs. For the circuit shown below (left),  $I_{in1} = 1\mu A$ ,  $I_{in2} = 3\mu A$ , and  $I_{in3} = 0.5\mu A$  and the initial voltage across the capacitor is 0 when  $t = 0$ . The plot of  $V_{out}(t)$  for time  $t$  from 0-10s is shown on the right. Note that  $\mu = 10^{-6}$ . What is the value of the capacitor for each value of  $I_{in}$ ? *Note: the initial voltage across the capacitor at time  $t = 0$  is 0V in all three cases.*



**Solution/Answer:** As shown in the left plot, the current source  $I_{in}$  is charging the unknown capacitor  $C$  over time, the charges on  $C$  at time  $t$  equals to the integral of current over time:  $Q_C(t) = \int I_{in} dt = I_{in} t$ . Therefore, we have  $u_+(t) = V_C(t) = \frac{Q_C(t)}{C} = \frac{I_{in} t}{C}$ . The turning point in the right graph is 6s, which means  $V_C(6s) = \frac{I_{in} 6s}{C} = u_+ = u_- = 3V$ .


$$I_{in1} C = I_{in} \frac{6s}{3V} = 2\mu F$$

$$I_{in2} C = I_{in} \frac{6s}{3V} = 6\mu F$$

$$I_{in3} C = I_{in} \frac{6s}{3V} = 1\mu F$$

## 2. Data Conversion Circuits

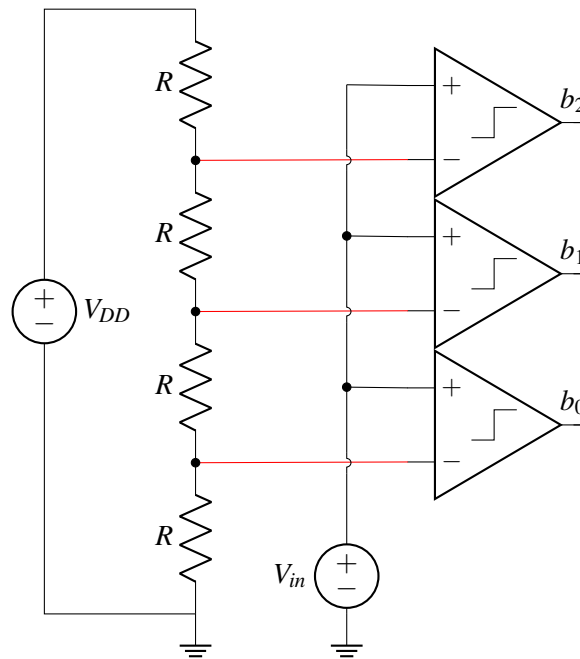- (a) The dual to DAC circuits are analog-to-digital converters, or ADC circuits. Here is an example of one, called a "Flash ADC," using resistors and comparators:



*Note: The red wires in the diagram are regular wires, but have been colored to show that they do not touch the crossing black wires.*

The resistor ladder gives us a set of reference voltages to compare against. We use a set of comparators to compare the input voltage  $V_{in}$  against these reference levels, and we get out a corresponding digital code  $b_0$ ,  $b_1$ , and  $b_2$ .

Assume that  $V_{DD} = 1\text{ V}$ , and that the comparators are connected to rails  $V_{DD} = 1\text{ V}$  and  $V_{SS} = 0\text{ V}$ . If  $V_{in}$  is  $0.3\text{ V}$ , **what are the outputs  $b_0$ ,  $b_1$ , and  $b_2$ ?**

**Solution/Answer:** The reference voltages for the comparators, from bottom to top, are  $\frac{1}{4}V_{DD} = 0.25\text{ V}$ ,  $\frac{1}{2}V_{DD} = 0.5\text{ V}$ , and  $\frac{3}{4}V_{DD} = 0.75\text{ V}$ . Each comparator checks if  $V_{in}$  is greater than the reference voltage, outputting  $V_{DD}$  if it is greater and  $V_{SS}$  if not. We are given  $V_{in} = 0.3\text{ V}$ , so  $b_0 = V_{DD} = 1\text{ V}$ ,  $b_1 = V_{SS} = 0\text{ V}$ ,  $b_2 = V_{SS} = 0\text{ V}$ .

If you left your answer in terms of 1s and 0s, i.e.  $b_0 = 1, b_1 = 0, b_2 = 0$ , that is valid too.