

# EECS 16A Designing Information Devices and Systems I Discussion 7B

## 1. Resist the Touch

Investigate the  $N \times N$  resistive touchscreen with vertical length  $L$  and horizontal width  $W$  shown in Figure 1. The touchscreen is constructed in two layers: a flexible conductive top layer comprised of  $N$  vertically oriented strips with even spacing  $\frac{W}{N+1}$ ; and a rigid conductive bottom layer comprised of horizontally oriented strips with even spacing  $\frac{L}{N+1}$ .

The vertical and horizontal strips form a grid of detectable touch points. The upper left touch point in Figure 1(b) is position  $(1, 1)$ , and the upper right touch point is  $(N, 1)$ . All strips in top and bottom layers have equal resistivity,  $\rho$ , and cross-sectional area,  $A$ .

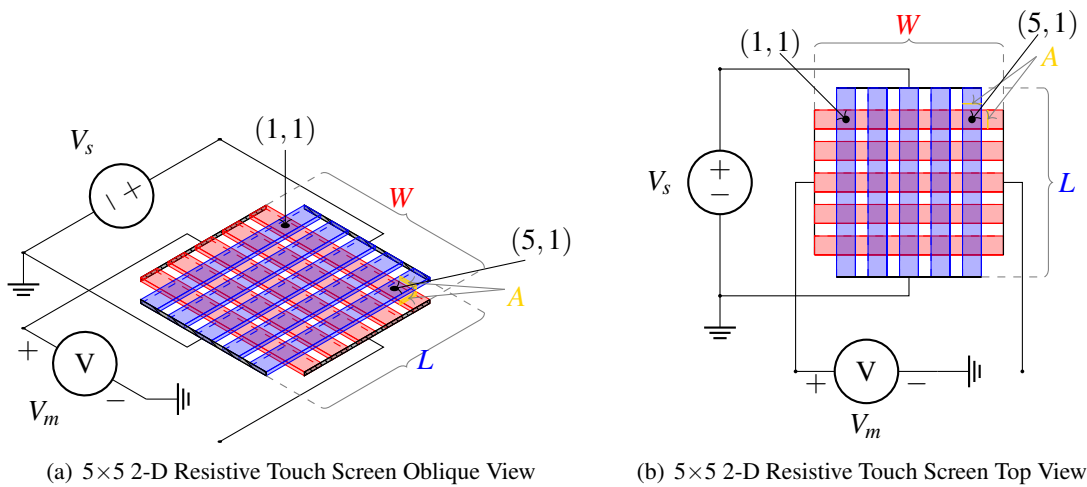


Figure 1:  $N \times N$  Resistive Touch Screen,  $N = 5$

- (a) Find the resistance  $R_y$  for a single vertical blue strip and  $R_x$  for a single horizontal red strip as a function of the screen dimensions  $W$  and  $L$ , the strip resistivity  $\rho$ , and the cross-sectional area  $A$ .

**Answer:**

The equation for resistance of a rectangular prism is  $R = \frac{\rho l}{A}$ , where  $\rho$  is the resistivity,  $l$  is the length, and  $A$  is the cross-sectional area.


Therefore for the horizontal (red, bottom layer) resistive strips we have,  $R_x = \frac{\rho W}{A}$ .

For the vertical (blue, top layer) resistive strips,  $R_y = \frac{\rho L}{A}$ .


- (b) Consider a  $2 \times 2$  example for the touchscreen circuit, as shown in Figure 2.

Assume a voltage source  $V_s$  is connected from the top to bottom terminals of all the vertical (blue) strips, and a voltmeter  $V_m$  is connected from the left terminal of all horizontal (red) strips to the negative terminal of the voltage source.

If  $V_s = 3\text{ V}$ ,  $R_x = 2000\Omega$ , and  $R_y = 2000\Omega$ , draw the equivalent circuit for when the point  $(2, 2)$  is pressed and solve for the measured voltage,  $V_m$ , with respect to ground.

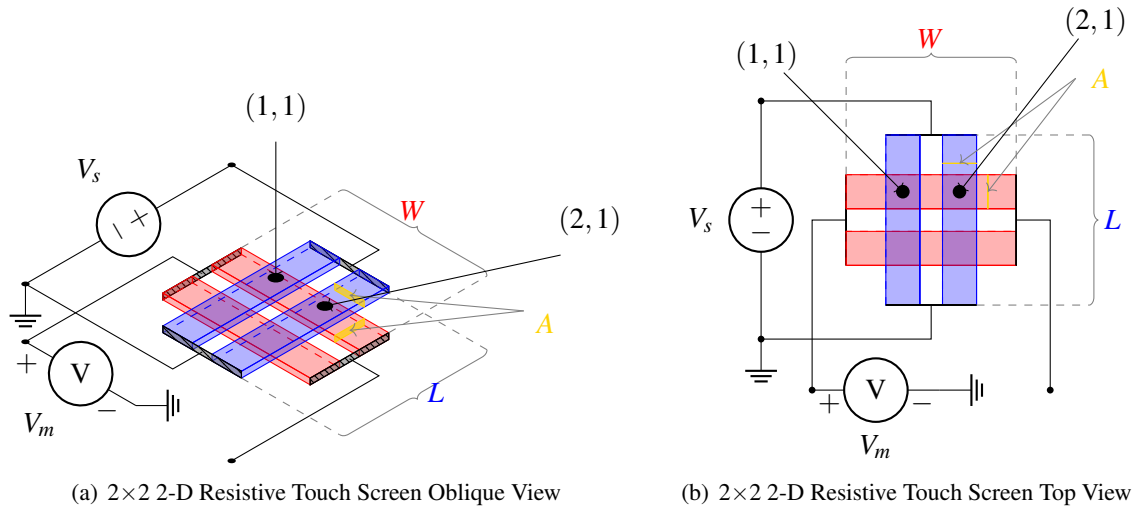
Figure 2:  $2 \times 2$  Resistive Touch Screen**Answer:**

All top layer strips and bottom layer strips are spaced apart equally, the upper left touch point is position  $(1, 1)$ , and the lower right touch point is  $(2, 2)$ . The spacing between the vertical (blue) strip centerlines in the top layer is  $\frac{W}{N+1}$ , and the spacing between the horizontal (red) strip centerlines in the bottom layer is  $\frac{L}{N+1}$ . Consequently, each strip can be effectively divided into  $N + 1$  equal length segments.

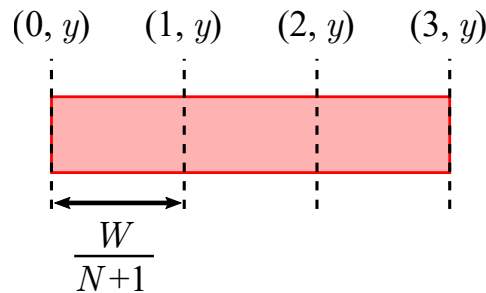


Since all of the resistive strips are equally spaced, the resistance above point  $(2, 2)$  on the top layer, vertical, blue strip becomes  $\rho \frac{\frac{2L}{3}}{A} = \frac{2}{3} \rho \frac{L}{A} = \frac{2}{3} R_y$  and the resistance below point  $(2, 2)$  on this vertical strip becomes  $\rho \frac{\frac{L}{3}}{A} = \frac{1}{3} \rho \frac{L}{A} = \frac{1}{3} R_y$ .

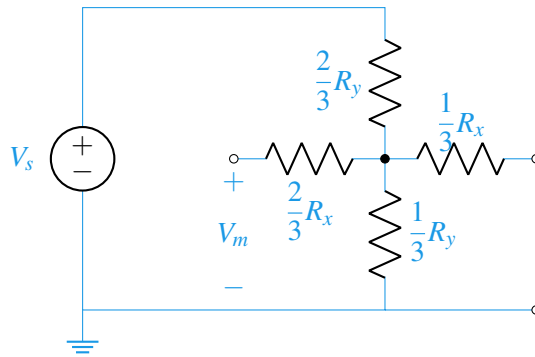A similar argument can be made for the horizontal (red, bottom layer) strip resistances  $R_x$ . However they do not affect the measured voltage,  $V_m$ , as they are terminated with equivalent open circuits, leading to no current flow and therefore no voltage drops.



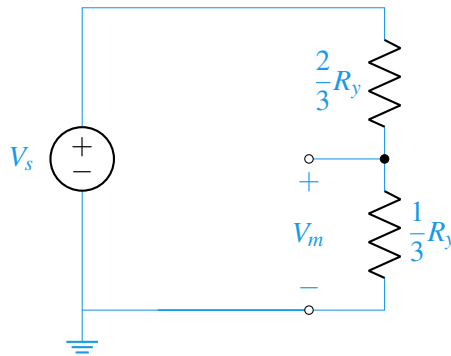Observing that the rightmost vertical (blue, top layer) resistive strip forms a voltage divider, and remembering that there is no voltage drop across the dangling  $R_x$  resistors we can write an equivalent circuit



and we can determine  $V_m$  using the voltage divider equation.


$$V_m = V_{(2,2)} = V_s \frac{\frac{1}{3}R_y}{\frac{1}{3}R_y + \frac{2}{3}R_y} = \frac{1}{3}V_s = 1\text{V}$$

Notice the measured voltage  $V_m$  does not depend on the actual strip resistances  $R_x$  and  $R_y$ .

- (c) Suppose a touch occurs at coordinates  $(i, j)$  for an arbitrary  $N \times N$  touchscreen, and the voltage source and meter are connected as in the diagrams. Find an expression for  $V_m$  as a function of  $V_s$ ,  $N$ ,  $i$ , and  $j$ .

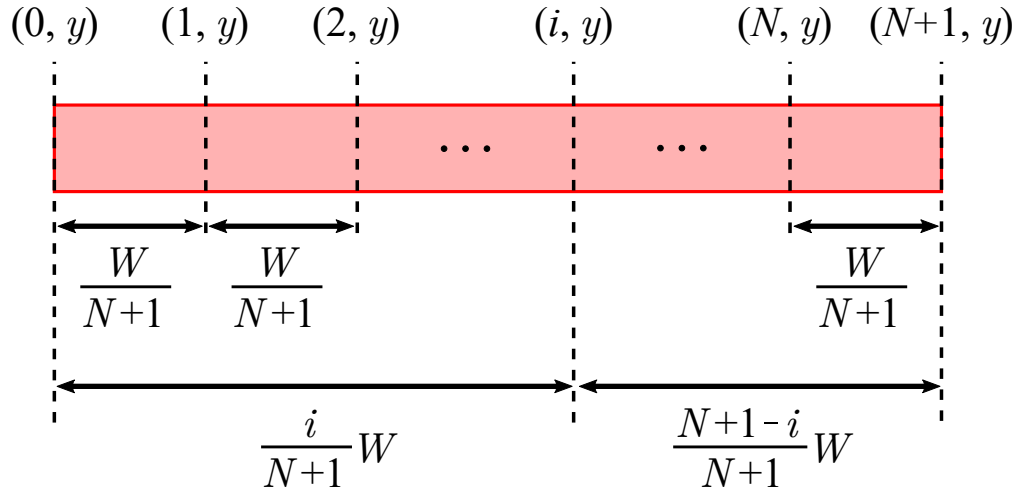**Answer:**

Just like for the 2x2 resistive touchscreen in part (b), the spacing between the vertical (blue) strip centerlines in the top layer is  $\frac{W}{N+1}$ , and the spacing between the horizontal (red) strip centerlines in the bottom layer is  $\frac{L}{N+1}$ . Consequently, each strip can be effectively divided into  $N + 1$  equal length segments.



The voltage does not depend on the  $x$  coordinate,  $i$ , as the voltmeter is connected to the ends of the dangling horizontal stripe (red). Just like in part (b), we will only be able to detect changes in the  $y$  coordinate. If the touch point occurs at  $(i, j)$ , the  $i$ -th vertical (blue) strip from the left will be split into lengths of  $L_{top} = \frac{j}{N+1}L$  and  $L_{bottom} = \frac{N+1-j}{N+1}L$  at the  $j$ -th touch point from the top. The voltmeter measures the voltage across the bottom half of the vertical (blue) resistance. We can also express the voltage divider directly as a ratio of the *lengths* of the resistances as

$$V_m = \frac{L_{bottom}}{L_{top} + L_{bottom}} V_s = \frac{L_{bottom}}{L} V_s = \frac{\frac{N+1-j}{N+1}L}{L} V_s = \frac{N+1-j}{N+1} V_s$$