

# EECS 16A      Designing Information Devices and Systems I

## Fall 2022      Discussion 8B

### 1. Superposition


For the following circuits, use the superposition theorem to solve for the voltages across the resistor(s).

#### Solution/Answer:

For each circuit;


- Redraw the circuits with just one source enabled (while disabling/zero-ing all other sources) and solve for circuit voltages and currents.
- Repeat for every independent source.
- Finally, linearly sum the circuit voltages and currents.

(a)

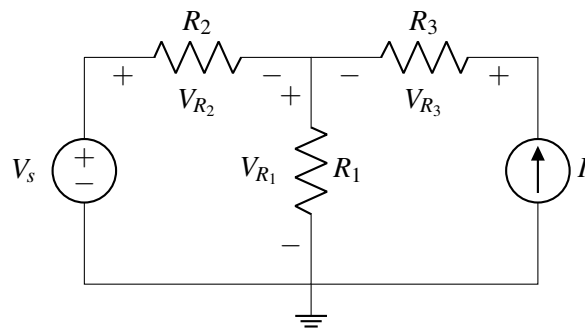
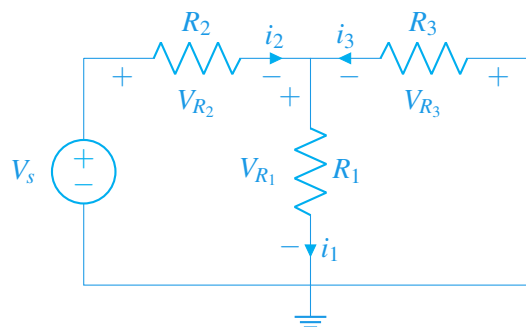
#### Answer:

Enable/turn-on only the voltage source,  $V_s$ , and disable/zero the current source ( $I_s = 0$  A so is equivalent to an open circuit). Because of the equivalent open circuit, no current flows through resistor  $R_3$  and it can be neglected. What is left is a classic resistive voltage divider.




$$V_{R_1} = \frac{R_1}{R_1 + R_2} V_s$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_s$$

$$V_{R_3} = 0$$

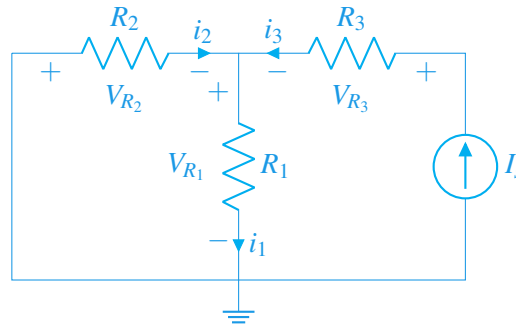Next, enable only the current source,  $I_s$ , and disable/zero the voltage source ( $V_s = 0$  V so is equivalent to a short circuit).



Intuitively, the current through  $R_3$  is  $I_s$  and then splits between  $R_1$  and  $R_2$ .

From element I-V characteristics (e.g., Ohm's Law), we know that  $V_{R_1} = i_1 R_1$ ,  $V_{R_2} = i_2 R_2$ , and  $I_s = i_3$ . We also know from KCL that  $i_2 + i_3 = i_1$ , and from KVL that  $V_{R_1} = -V_{R_2}$ .

If we solve this system, for  $V_{R_1}$  we find

$$i_3 = i_1 - i_2$$

$$I_s = \frac{V_{R_1}}{R_1} - \frac{V_{R_2}}{R_2}$$

$$I_s = \frac{V_{R_1}}{R_1} + \frac{V_{R_1}}{R_2}$$

$$I_s = V_{R_1} \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow V_{R_1} = \frac{R_1 R_2}{R_1 + R_2} I_s$$

for  $V_{R_2}$  we find

$$V_{R_2} = -V_{R_1} = -\frac{R_1 R_2}{R_1 + R_2} I_s$$

and for  $V_{R_3}$

$$V_{R_3} = i_3 R_3 = I_s R_3$$

The unknown branch currents  $i_1$  and  $i_2$  can also be quickly found. They could also have been derived from recognizing the circuit as a current divider between  $R_1$  and  $R_2$ .

$$i_1 = \frac{R_2}{R_1 + R_2} I_s$$

$$i_2 = -\frac{R_1}{R_1 + R_2} I_s$$


Finally, using superposition we can sum up the contributions from both  $V_s$  and  $I_s$  to find the resistor voltages of the complete circuit

$$V_{R_1} = V_{R_1} \Big|_{I_s=0} + V_{R_1} \Big|_{V_s=0} = \frac{R_1}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$V_{R_2} = V_{R_2} \Big|_{I_s=0} + V_{R_2} \Big|_{V_s=0} = \frac{R_2}{R_1 + R_2} V_s - \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$V_{R_3} = V_{R_3} \Big|_{I_s=0} + V_{R_3} \Big|_{V_s=0} = I_s R_3$$

(b)

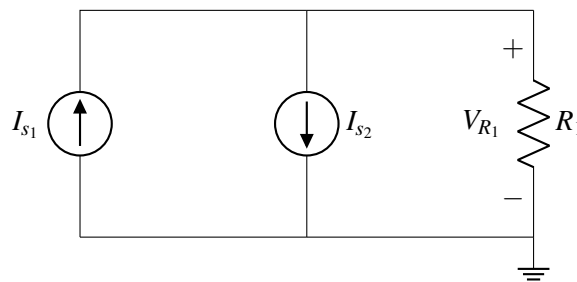

**Answer:**

i. *Using superposition:*

Enabling  $I_{s1}$  (and disabling  $I_{s2}$ ) gives  $V_{R_1} = I_{s1} R_1$ . Enabling  $I_{s2}$  (and disabling  $I_{s1}$ ) gives  $V_{R_1} = -I_{s2} R_1$ . Finally, the total  $V_{R_1}$  is the sum of the individual  $V_{R_1}$ 's or


$$V_{R_1} = (I_{s1} - I_{s2}) R_1$$

ii. *Without superposition:*

Let's approach this holistically. We're looking for the voltage across the resistor, which could be found quickly using Ohm's law if we knew the current. If we were to apply KCL at the node at the top of the circuit, one source is coming in, the other source is leaving, and the current through the resistor is leaving. From KCL, we then know  $i_{R_1} = I_{s1} - I_{s2}$ . Applying Ohm's Law we find:

$$V_{R_1} = (I_{s1} - I_{s2}) R_1$$

(c) **(PRACTICE)**

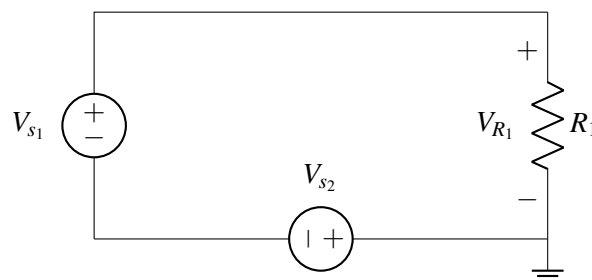

**Answer:**

i. *Using superposition:*

Enabling  $V_{s1}$  (and disabling  $V_{s2}$ ) gives  $V_{R1} = V_{s1}$ . Enabling  $V_{s2}$  (and disabling  $V_{s1}$ ) gives  $V_{R1} = -V_{s2}$ . Finally, the total  $V_{R1}$  is the sum of the individual  $V_{R1}$ 's or

$$V_{R1} = V_{s1} - V_{s2}$$


ii. *Without superposition:*

Notice the circuit only has one loop, so use KVL to find the voltage across the resistor.

$$V_{R1} = V_{s1} - V_{s2}$$

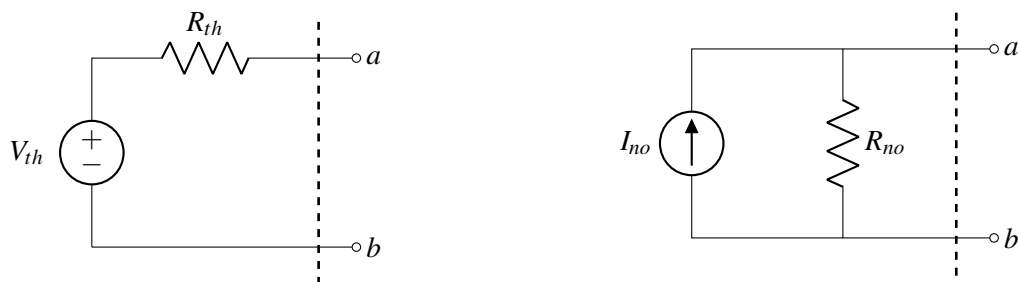
## 2. Thévenin and Norton Equivalence

The general Thévenin and Norton equivalent circuits are shown below:



Find the Thévenin and Norton equivalents across terminals  $a$  and  $b$  for the circuits given below.

(a)

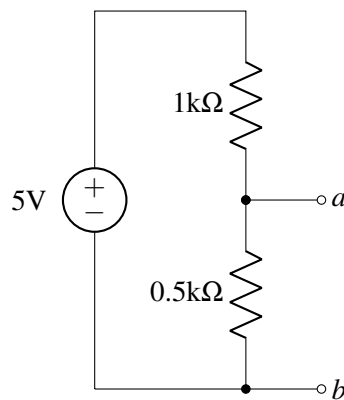


### Answer:

To find  $V_{th}$ , simply find the open circuit voltage across terminals  $ab$ . Here, that voltage is the voltage across the 0.5kΩ resistor given by the voltage divider equation.

$$V_{th} = 5V \frac{0.5k\Omega}{1k\Omega + 0.5k\Omega} = 1.67V$$

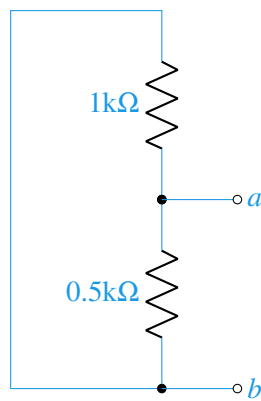To find  $R_{th}$ , disable/zero out any independent sources (5V voltage source becomes a short circuit).




Then, from the open circuit terminals  $ab$ , find the equivalent resistance of the rest of the circuit. This is just two resistors in parallel. Elements or groups of elements are in parallel if their terminals share the same two nodes (i.e., have same voltage across them).

$$R_{th} = 1\text{ k}\Omega \parallel 0.5\text{ k}\Omega = \frac{1\text{ k}\Omega \cdot 0.5\text{ k}\Omega}{1\text{ k}\Omega + 0.5\text{ k}\Omega} = 333\ \Omega$$

Note that  $R_{th} = R_{no}$  always. Now to find  $I_{no}$ ,

$$I_{no} = \frac{V_{th}}{R_{th}} = \frac{1.67\text{ V}}{333\ \Omega} = 5\text{ mA}$$

(b)

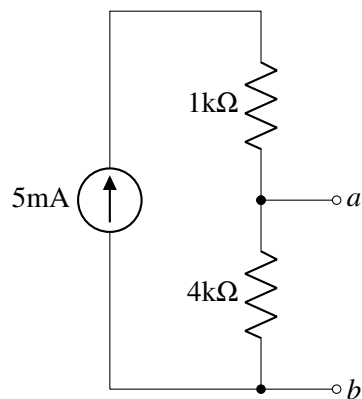


**Answer:**

The open circuit voltage across terminals  $ab$  is given by Ohm's law:

$$V_{th} = 5\text{ mA} \cdot 4\text{ k}\Omega = 20\text{ V}$$

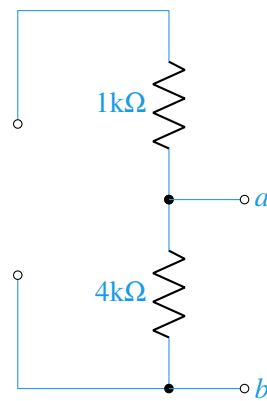To find  $R_{th}$ , disable/zero out any independent sources (5A current source becomes an open circuit).



Then, from the open circuit terminals  $ab$ , find the equivalent resistance of the rest of the circuit. This is just a single resistor.

$$R_{th} = 4\text{k}\Omega = R_{no}$$

Now to find  $I_{no}$ ,

$$I_{no} = \frac{V_{th}}{R_{th}} = \frac{20\text{ V}}{4\text{k}\Omega} = 5\text{ mA}$$