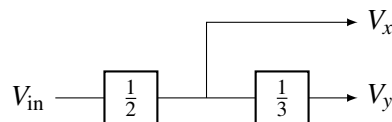


# EECS 16A      Designing Information Devices and Systems I

## Fall 2022      Discussion 11A

### 1. Modular Circuit Buffer

Let's try designing circuits that perform a set of mathematical operations using op-amps. While voltage dividers on their own cannot be combined without altering their behavior, op-amps can preserve their behavior when combined and thus are a perfect tool for modular circuit design. We would like to implement the block diagram shown below:



In other words, create a circuit with two outputs  $V_x$  and  $V_y$ , where  $V_x = \frac{1}{2}V_{in}$  and  $V_y = \frac{1}{3}V_x = \frac{1}{6}V_{in}$ .

- (a) Draw two voltage dividers, one for each operation (the  $1/2$  and  $1/3$  scalings). What relationships hold for the resistor values for the  $1/2$  divider, and for the resistor values for the  $1/3$  divider?

**Answer:** Recall our voltage divider consists of  $V_{in}$  connected to two resistors ( $R_1, R_2$ ) in series with the output voltage between ground and the central node. This yields the formula


$$V_{out} = \left( \frac{R_2}{R_1 + R_2} \right) V_{in}.$$

For the  $1/2$  operation ( $V_x$  output) we recognize


$$\frac{1}{2} = \left( \frac{R_2}{R_1 + R_2} \right) \longrightarrow R_1 + R_2 = 2R_2 \longrightarrow R_1 = R_2 \equiv R_x.$$

For the  $1/3$  operation ( $V_y$  output) we recognize
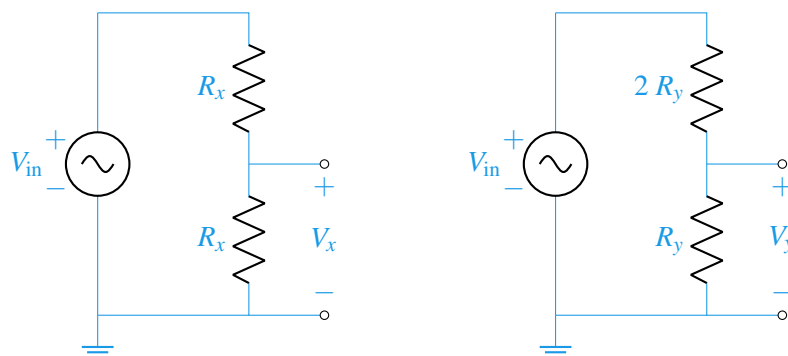
$$\frac{1}{3} = \left( \frac{R_2}{R_1 + R_2} \right) \longrightarrow R_1 + R_2 = 3R_2 \longrightarrow \frac{R_1}{2} = R_2 \equiv R_y.$$



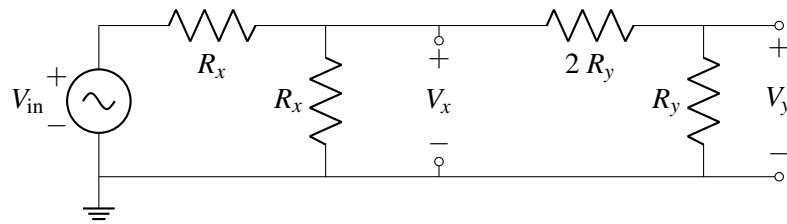- (b) If you combine the voltage dividers, made in part (a), as shown by the block diagram (output of the  $1/2$  voltage divider becomes the source for the  $1/3$  voltage divider circuit), do they behave as we hope (meaning  $V_{in} = 2V_x = 6V_y$ )?



**Answer:** To quickly access this combined system, we may identify  $V_x$  as the result of a new equivalent voltage divider (recognizing the  $R_y$  resistors in series and that series is in parallel with  $R_x$ ). The load resistor becomes  $R_{eq} = \frac{3R_x R_y}{R_x + 3R_y}$ . This yields

$$V_x = \left( \frac{R_{eq}}{R_x + R_{eq}} \right) V_{in} = \left( \frac{1}{2 + \frac{R_x}{3R_y}} \right) V_{in} \quad V_y = \frac{1}{3} V_x = \left( \frac{1}{6 + \frac{R_x}{R_y}} \right) V_{in}$$

From this stage it is evident that combining our dividers changes their behavior (although they preserve behavior in the limit  $R_y \gg R_x$ ).

The new values for  $V_x, V_y$  are dependent on values from both dividers, which means they can't be treated independently!  $\square$ .


(c) Perhaps we could use an op-amp (in negative-feedback) to achieve our desired behavior.

Modify the implementation you tried in part (b) using a negative feedback op-amp in order to achieve the desired  $V_x, V_y$  relations  $V_x = \frac{V_{in}}{2}$  and  $V_y = \frac{V_x}{3} = \frac{V_{in}}{6}$ .

HINT: Place the op-amp in between the dividers such that the  $V_x$  node is an input into the op-amp, while the source of the 2nd divider is the output of the op-amp!

**Answer:** Use the op-amp as a voltage buffer.

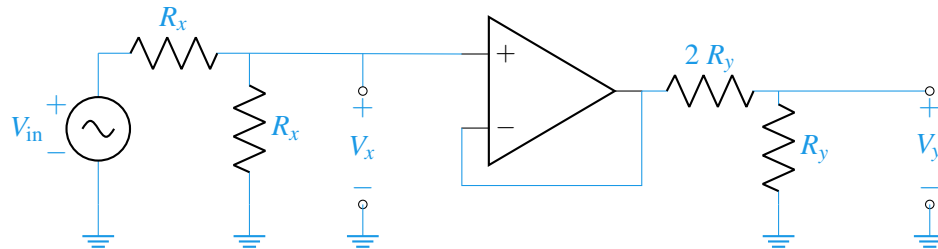
This means we short the op-amp's negative input to its output, since the positive input must now match its output (by the golden rules).



Since no current flows into the positive op-amp input, we've successfully isolated the dividers so they can be used in a modular fashion! □


NOTE: The  $V_x, V_y$  outputs from this configuration would change with the addition of a load on either terminal. As a follow-up, think about ways to make each output agnostic to the loads attached!

## 2. Multiple Inputs To One Op-Amp

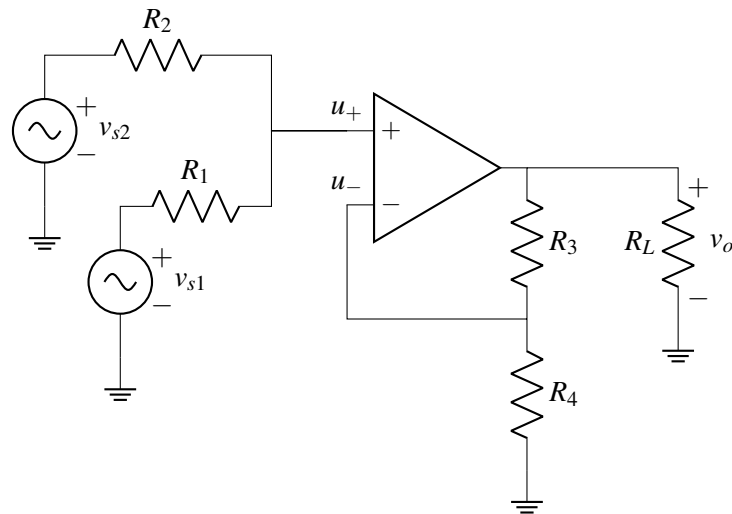

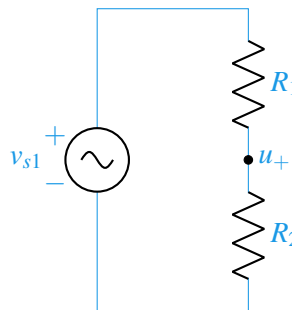- (a) First, let's focus on the left part of the circuit containing the voltage sources  $v_{s1}$  and  $v_{s2}$ , and resistances  $R_1$  and  $R_2$ . Solve for  $u_+$  in the circuit above. (Hint: Use superposition.)


**Answer:** Let's call the potential at the positive input of the op-amp  $u_+$ . Using superposition, we first turn off  $v_{s2}$  and find  $u_+$ . The circuit then looks like:



We recognize the above circuit as a voltage divider. Thus,

$$u_{+,vs1} = \frac{R_2}{R_1 + R_2} v_{s1}$$

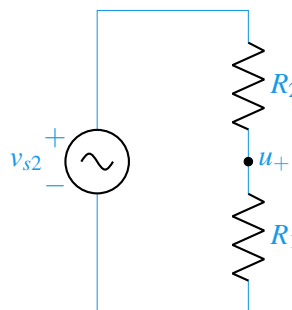By symmetry, we expect  $v_{s2}$  to have a similar circuit and expression. The circuit for  $v_{s2}$  looks like:



The expression for  $u_+$  with  $v_{s2}$  is then:

$$u_{+,vs2} = \frac{R_1}{R_1 + R_2} v_{s2}$$

From superposition, we know the output must be the sum of these.

$$u_+ = \frac{R_2}{R_1 + R_2} v_{s1} + \frac{R_1}{R_1 + R_2} v_{s2}$$

- (b) How would you choose  $R_1$  and  $R_2$  that produce a voltage  $u_+ = \frac{1}{2}V_{s1} + \frac{1}{2}V_{s2}$ ? Could you also achieve  $u_+ = \frac{1}{3}V_{s1} + \frac{2}{3}V_{s2}$ ?

**Answer:**

We found that the output voltage for any two resistors  $R_1$  and  $R_2$  is:

$$v_+ = \frac{R_2}{R_1 + R_2}V_1 + \frac{R_1}{R_1 + R_2}V_2$$

Thus, to create the  $\frac{1}{2} - \frac{1}{2}$  ratio, we can use any nonzero resistances with value  $R$  such that:

$$R_1 = R \quad R_2 = R$$

Similarly, to create the  $\frac{1}{3} - \frac{2}{3}$  ratio, we can use:

$$R_1 = 2R \quad R_2 = R$$

In general, you can achieve anything of the form  $u_+ = kV_1 + (1-k)V_2$  with  $k \in (0, 1)$ ! This is a very useful topology to combine two voltages.

- (c) Now, for the whole circuit, find an expression for  $v_o$ .

**Answer:**

With  $u_+$  determined, we can find the output voltage directly from the formula for a non-inverting amplifier. We can also derive it using the process below.

From the negative feedback rule,  $u_+ = u_-$ . Using voltage dividers, we can express  $u_-$  in terms of  $v_o$ :

$$u_- = \frac{R_4}{R_3 + R_4}v_o$$

$$v_o = \left(1 + \frac{R_3}{R_4}\right)u_- = \left(1 + \frac{R_3}{R_4}\right)u_+$$

Now, to find the final output, we can set  $u_+$  to our earlier expression.

$$v_o = \left(1 + \frac{R_3}{R_4}\right) \left( \frac{R_2}{R_1 + R_2}v_{s1} + \frac{R_1}{R_1 + R_2}v_{s2} \right)$$

- (d) How could you use this circuit to find the sum of different signals, i.e.  $V_{s1} + V_{s2}$ ? What about taking the sum and multiplying by 2, i.e.  $2(V_{s1} + V_{s2})$ ?

**Answer:**

The circuit already finds the weighted sum of two inputs. By setting  $R_1 = R_2$  and  $R_3 = R_4$ , we can take the exact sum of two inputs.

$$v_o = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{R_2}{R_1 + R_2} v_{s1} + \frac{R_1}{R_1 + R_2} v_{s2}\right) = (1 + 1) \left(\frac{1}{2} v_{s1} + \frac{1}{2} v_{s2}\right) = v_{s1} + v_{s2}$$

Notice that the first half of this circuit ( $R_1$  and  $R_2$ ) form a voltage summer with coefficients less than one; the second half is just a non-inverting amplifier. Thus we can always use  $R_1$  and  $R_2$  to take an equally weighted sum of the inputs and then multiply greater than 1 using the non-inverting amplifier. If we set  $R_1 = R_2$ , we get  $\left(\frac{1}{2} v_{s1} + \frac{1}{2} v_{s2}\right)$  into the op-amp. To get a total gain of 2, then the non-inverting op-amp needs a gain of 4, so we can pick  $R_3 = 3R_4$ .


### 3. (Optional) Designing a Current Divider

- (a) You have two current sources,  $I_1$  and  $I_2$ . You also have a load resistor  $R_L = 6\text{ k}\Omega$ . You can use whatever resistors you want (as long as they are finite integer multiples of  $1\text{ k}\Omega$ ). How would you design a circuit such that the current running through  $R_L$  is  $I_L = \frac{2}{5}(I_1 + I_2)$ ?

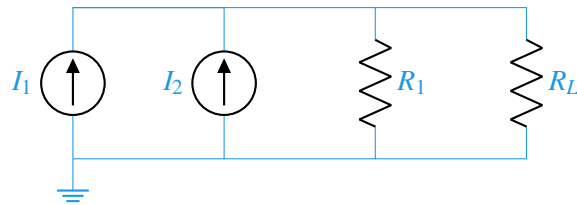**Answer:**

Use superposition, so think of the two currents as one summed current. Then, use KCL to determine how to divide the currents. Remember, the current divider formula is similar to that of the voltage divider, with the numerators flipped. This means that in the current divider, when calculating the current through one resistor we place the other resistor in the numerator, i.e.:

$$I_{R1} = \frac{R_L}{R_1 + R_L} (I_1 + I_2), \quad I_{R_L} = \frac{R_1}{R_1 + R_L} (I_1 + I_2)$$



Using the above equations, we get that one possible resistor combination that creates  $I_L = \frac{2}{5}(I_1 + I_2)$  is:

$$R_L = 6\text{ k}\Omega, R_1 = 4\text{ k}\Omega$$