


# EECS 16A      Designing Information Devices and Systems I

## Fall 2022      Discussion 6B

### 1. Passive Sign Convention and NVA Basics

The following question is a modified version of Spring 2022 Midterm 2 Question 1


Suppose we have the following circuit:

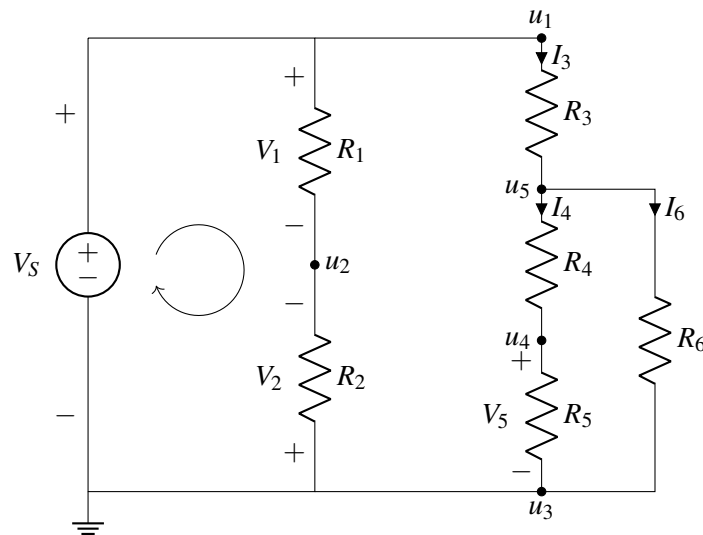

- Following passive sign convention, **label** the missing currents and the missing voltages for each element in the circuit, including the voltage source.
- Write the KCL expression** at node  $u_5$  in terms of currents  $I_3$ ,  $I_4$ , and  $I_6$  as labeled in the circuit diagram.
- Find the voltage across  $R_4$ ,  $R_5$ , and  $R_6$  in terms of the node voltages  $u_3$ ,  $u_4$ , and  $u_5$ . Then use Ohm's law to express the currents across  $R_4$ ,  $R_5$ , and  $R_6$  in terms of node voltages and resistances.
- (OPTIONAL) **Write the KVL expression** for the loop drawn in the circuit diagram in terms of voltages  $V_S$ ,  $V_1$ , and  $V_2$ .
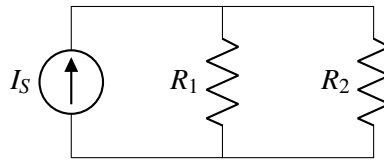
## 2. A Simple Current Circuit


For the circuit shown below, find the voltages across all the elements and the currents through all the elements.



- (a) In the above circuit, pick a reference node. Does your choice of reference matter?

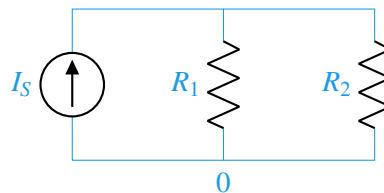**Answer:**


There are two nodes in this circuit and thus two choices for the reference node. The choice of reference does not matter. We will use the reference node shown below:



- (b) With your choice of reference, label the node potentials for every node in the circuit.

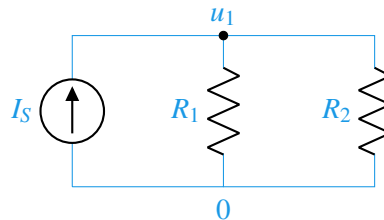**Answer:**


Since this circuit only has two nodes, there will only be one additional node potential.



- (c) Label all of the branch currents. Does the direction you pick matter?

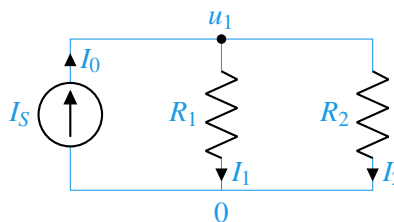**Answer:**


When labeling the currents through branches, the direction you pick does not matter.



- (d) Draw the  $+/-$  labels on every element. What convention must you follow?

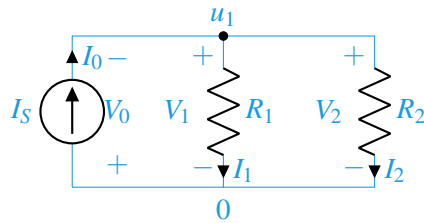**Answer:**

When drawing the  $+/-$  labels, you must follow the passive sign convention. That is, current flows into the  $+$  terminal of every element.



(e) Use KCL to find as many equations as you can.

**Answer:**

KCL gives us one equation for the node at the top, namely that  $I_0 - I_1 - I_2 = 0$ .

(f) Use KVL and Ohm's law to find the remaining equations to solve the circuit.

**Answer:** We know that the current through the current source must be the value of the current source, i.e.

$$I_0 = I_S \quad (1)$$

We also know that the voltage across the resistor is equal to the current times the resistance, i.e.

$$\begin{aligned} V_1 &= I_1 R_1 \\ V_2 &= I_2 R_2 \end{aligned} \quad (2)$$

Writing the equations for node potentials we have:

$$\begin{aligned} 0 - u_1 &= V_0 \\ u_1 - 0 &= V_1 \\ u_1 - 0 &= V_2 \end{aligned} \quad (3)$$

Using Equation (5) and substituting expressions from Equation (6) into Equation (7), we have:

$$\begin{aligned} I_0 &= I_S \\ V_1 = I_1 R_1 &\implies I_1 = \frac{u_1}{R_1} \\ V_2 = I_2 R_2 &\implies I_2 = \frac{u_1}{R_2} \end{aligned} \quad (4)$$

(g) Solve for the voltages across both resistors and the currents going through them if  $I_S = 5 \text{ A}$ ,  $R_1 = 5 \Omega$ , and  $R_2 = 10 \Omega$ .

**Answer:** Substituting what we found from the last two parts, we have:

$$\begin{aligned} I_0 - I_1 - I_2 &= 0 \\ I_S - \frac{u_1}{R_1} - \frac{u_1}{R_2} &= 0 \\ I_S &= u_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \\ 5 &= u_1 \left( \frac{1}{5} + \frac{1}{10} \right) \\ u_1 &= \frac{5}{\frac{1}{5} + \frac{1}{10}} \\ u_1 &= 16.67 \text{ V} \end{aligned} \quad (5)$$

Therefore  $V_1 = V_2 = u_1 = 16.67$  V. Now to solve for currents going through each resistor, we just plug in  $u_1$  back into equations we found, so:

$$\begin{aligned} I_1 &= \frac{u_1}{R_1} = 3.33A \\ I_2 &= \frac{u_1}{R_2} = 1.67A \end{aligned} \quad (6)$$

- (h) (OPTIONAL) Rather than solve for the system using substitution, we can also use matrices! Set up a matrix equation in the form  $\mathbf{A}\vec{x} = \vec{b}$  to solve for the unknown node potentials and currents, which are  $I_0, I_1, I_2$  and  $u_1$ . Then use part (e) and (f) to fill in the entries of  $\mathbf{A}$  and  $\vec{b}$ , and solve for the unknowns.

**Answer:**

$$\begin{bmatrix} ? & ? & ? & ? \\ ? & ? & ? & ? \\ ? & ? & ? & ? \\ ? & ? & ? & ? \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} ? \\ ? \\ ? \\ ? \end{bmatrix}$$

$\mathbf{A}$  will be a  $4 \times 4$  matrix since there are four unknowns in the circuit, the currents  $I_0, I_1$ , and  $I_2$  and the one potential  $u_1$ .

We then fill in the KCL equations into the matrix as follows:

$$\begin{bmatrix} 1 & -1 & -1 & 0 \\ ? & ? & ? & ? \\ ? & ? & ? & ? \\ ? & ? & ? & ? \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} 0 \\ ? \\ ? \\ ? \end{bmatrix}$$

Then we fill in the rest of the matrix with Ohm's Law equations. Note that we need to rearrange the equations, so  $I_1 = \frac{u_1}{R_1} \implies I_1 R_1 - u_1 = 0$  and  $I_2 = \frac{u_1}{R_2} \implies I_2 R_2 - u_1 = 0$ .

$$\begin{bmatrix} 1 & -1 & -1 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & -R_1 & 0 & 1 \\ 0 & 0 & -R_2 & 1 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} 0 \\ I_S \\ 0 \\ 0 \end{bmatrix}$$

By plugging in the values we are given into the system of equations, we get:

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \\ u_1 \end{bmatrix} = \begin{bmatrix} 5 \\ 3.33 \\ 1.67 \\ 16.67 \end{bmatrix}$$